



**Faculty of Engineering and Technology  
Computer Systems Engineering Department**

**ADVANCED DIGITAL SYSTEMS DESIGN  
ENCS3310**

**Homework 2**  
**Designing sequential circuits**

**Prepared by:**  
**Abdel Rahman Shahan 1211753**

**Instructor:**  
**Dr. Abdallatif Abuissa**

**Section: 2**  
**Date: 6/7/2024**

- 1) Given the following primitive flow table, go through design procedure steps and implement the circuit using SR latches. [20 points]

Stable State	Inputs		output	Notes
	x1	x2	Q	
a	1	1	1	After c
b	0	1	0	After e
c	0	1	1	After a, f
d	1	0	0	After a, e, f
e	1	1	0	After b, d
f	0	0	1	After b, c, d

Step 1: translating primitive flow table

State/input	00	01	11	10
a	_, _	c, _	a, 1	d, _
b	f, _	b, 0	e, _	_, _
c	f, _	c, 1	a, _	_, _
d	f, _	_, _	e, _	d, 0
e	_, _	b, _	e, 0	d, _
f	f, 1	c, _	_, _	d, _

step 2: finding how many state variables we have:

count (a, b, c, d, e, f) = 6  $\rightarrow$   $\text{ceil}(\ln 6 / \ln 2) = 3$ . So, we need 3 state variables to implement this logic


step 3: now let's construct the table of reduction to reduce our state variables

b	c,b <del>a,e</del>				
c	✓	✗			
d	<del>a,e</del>	✓	<del>a,e</del>		
e	<del>b,c</del> a,e	✓	c,b <del>a,e</del>	✓	
f	✓	<del>b,c</del>	✓	✓	<del>b,c</del>
states	a	b	c	d	e

compatible pairs:

(a, c) (a, f) (b, d) (b, e) (c, f) (d, e) (d, f)

 step 4: now we use merger diagram to see what pairs we still have:



we can take (b, e, d) and (a, f, c) and (d, f)

since we already cover a and f in the first two states we don't need them. Now we remain with states:

(b, e, d) let's call it A

(a, f, c) let's call it B

step 5: creating new table with new states

state/input	00	01	11	10
b, e, d	f, _	b,0	e,0	d,0
a, f, c	f,1	c,1	a,1	d, _

using this table: we can fill the above table:

State/input	00	01	11	10
a	_, _	c, _	a,1	d, _
b	f, _	b,0	e, _	_, _
c	f, _	c,1	a, _	_, _
d	f, _	_, _	e, _	d,0
e	_, _	b, _	e,0	d, _
f	f,1	c, _	_, _	d, _

new table with replaced state names:

state/input	00	01	11	10
A	B, _	A,0	A,0	A,0
B	B,1	B,1	B,1	A, _

our table reduced flow table is now ready

step 6: state assignment and table separating output and next State

output Q table:

state/input	00	01	11	10
0	—	0	0	0
1	1	1	1	—

$1 \rightarrow 0: x$  |   
  $0 \rightarrow 1: x$  |   
  $0 \rightarrow 0: 0$  |   
  $1 \rightarrow 1: 1$

state/input	00	01	11	10
0	X	0	0	0
1	1	1	1	X

$Q = y$

next state table Y:

state/input	00	01	11	10
0	1	0	0	0
1	1	1	1	0

$$Y = (x_1' x_2') + (y x_2)$$

step 7: SR tables for Y

we need to use SR excitation table:

y	Y	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

S

state/input	00	01	11	10
0	1	0	0	0
1	x	x	x	0

R

state/input	00	01	11	10
0	0	x	x	x
1	0	0	0	1

$$S = (X1' X2')$$

$$R = (X1 X2')$$

Finally, we have:

$$Q = y$$


$$SY = (X1' X2')$$

$$RY = (X1 X2')$$



step 8: designing circuit

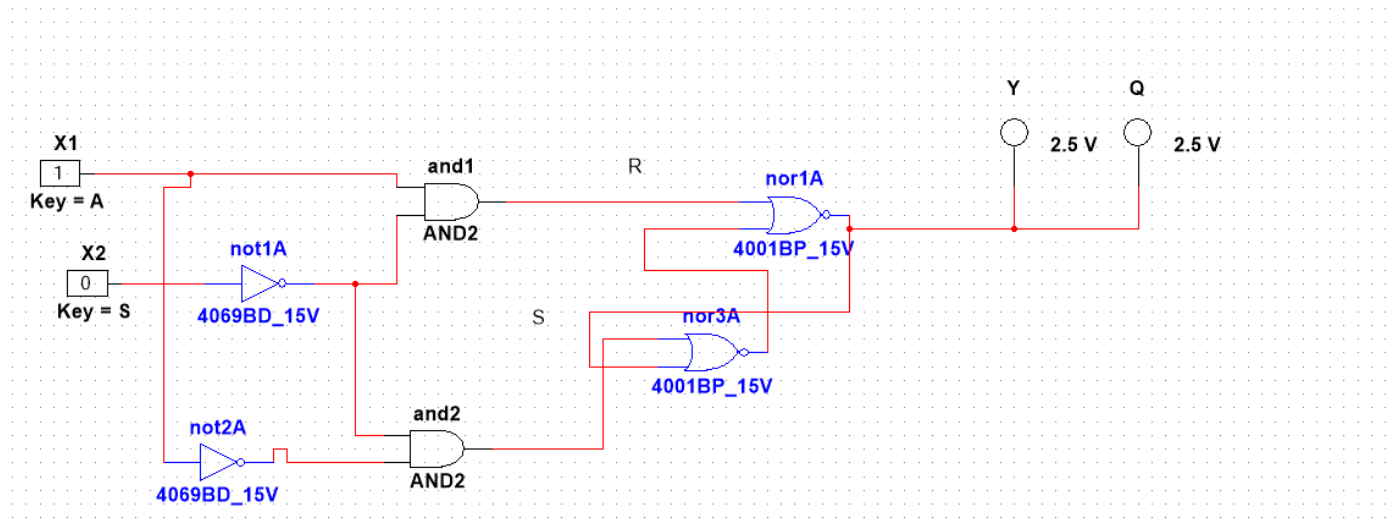personally, I prefer using NI Multisim 14.1



2) Show the primitive flow table for positive edge T-FF [10 points]

State	Inputs		Output	Comments
	$T$	$C$	$Q$	
$a$	1	0	0	After state d or f
$b$	1	1	1	After state a or g
$c$	1	0	1	After state b or h
$d$	1	1	0	After state c or e
$e$	0	1	0	After state d or f
$f$	0	0	0	After state a or e
$g$	0	1	1	After state b or h
$h$	0	0	1	After state c or g

2 laws:

- No more than 1 input change.
- $Q(t) = Q(t-1) \text{ ' @ } C: 0 \rightarrow 1 \text{ else } Q(t) = Q(t-1) \text{ (no change)}$

final primitive flow table:

State/input	00	01	11	10
a	f, _	_, _	b, _	a, 0
b	_, _	g, _	b, 1	c, _
c	h, _	_, _	d, _	c, 1
d	_, _	e, _	d, 0	a, _
e	f, _	e, 0	d, _	_, _
f	f, 0	e, _	_, _	a, _
g	h, _	g, 1	b, _	_, _
h	h, 1	g, _	_, _	c, _