

Post-lap

Experiment No. 2 - Comparators,
Adders, and Subtractors

*Student name: Abdulrahman
shaheen.

* ID#: 1211753.

* Instructor Name: Dr. Qadri Mayyala

* Date: 4/12/2023.

* Section: 2.

Q1) Design 8-bit BCD adder.


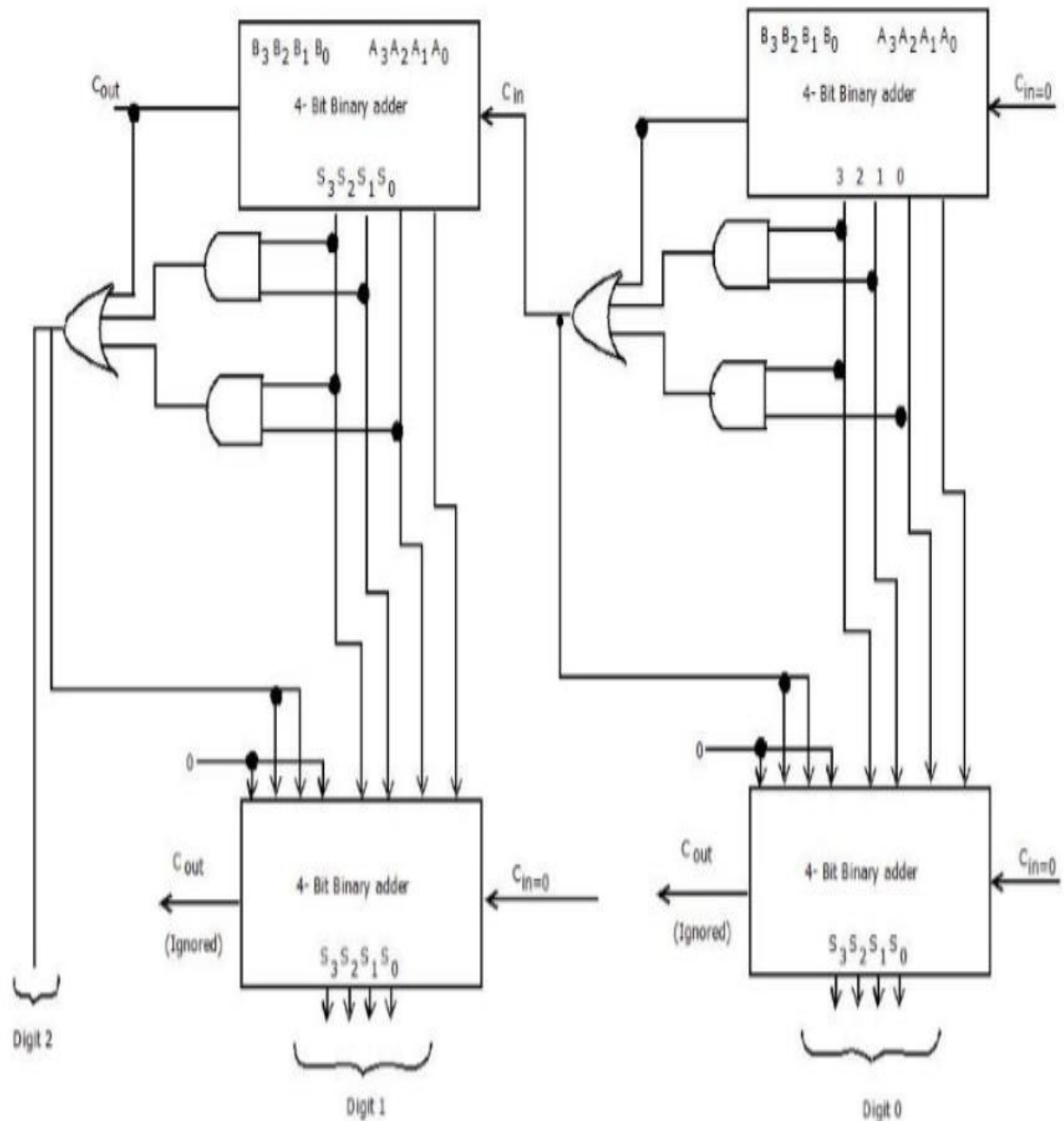


Fig : 8 - Bit BCD Adder

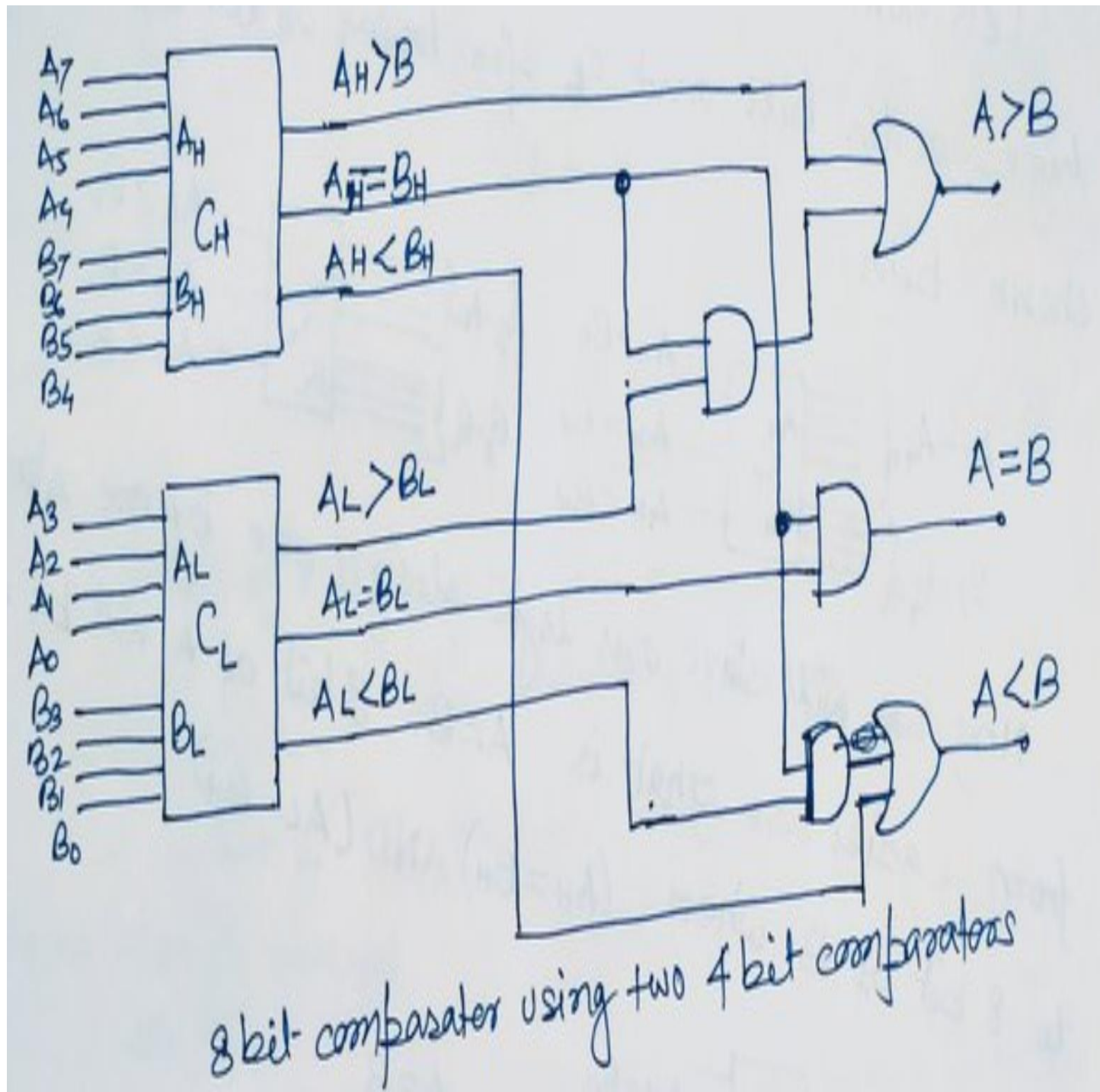Q2) Design 8-bit comparator using 2 of 4-bit comparator.



Q3) A 4-inputs, 3-outputs circuit that compares 2-bit unsigned numbers and outputs a '1' on one of three output lines according to whether the first number is greater than, equal to, or less than the other number. You can only use two 4×1 multiplexer.

Truth Table of 2-Bit Magnitude Comparator

INPUT				OUTPUT		
A1	A0	B1	B0	A>B	A=B	A<B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

